

Probability Hardware Assignment

Name -: Uttam Paharia
Roll no -: CS22BTECH11060

Abstract—In this assignment we have made a Random number generator using shift registers

COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE I
COMPONENTS USED

PROCEDURE

- 1) Connect the 555 timer circuit as shown in Figure 1.

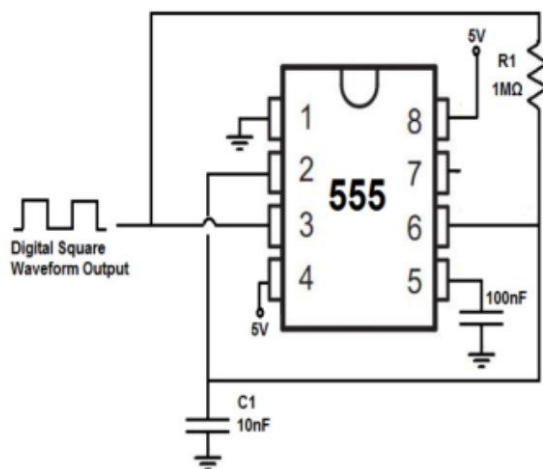


Fig. 1. Connection in 555 timer circuit

- 2) Connect the output of D flip-flops.
- 3) Perform the shifting of resistors using 4 D flip-flops (using two 7474 ICs).

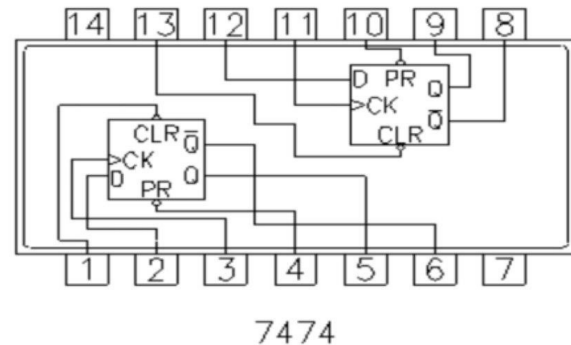


Fig. 2. Connection in 7474 IC

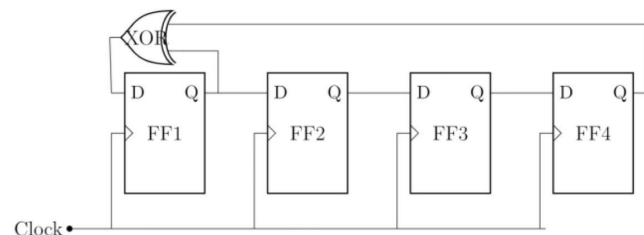


Fig. 3. Connection in XOR gate

- 4) Use XOR gate to obtain the result.
- 5) Connect the decoder (7447 IC) and link its inputs A, B, C, and D to Q_0 , Q_1 , Q_2 , and Q_3 outputs, respectively, as shown in Figure 4.



Fig. 4. Connection in Decoder gate

- 6) Connect the seven-segment display and connect it to the decoder (7447 IC) based on the connections specified in Table 5 and the figure in Figure 6.

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 5. Connection of seven-segment display with decoder

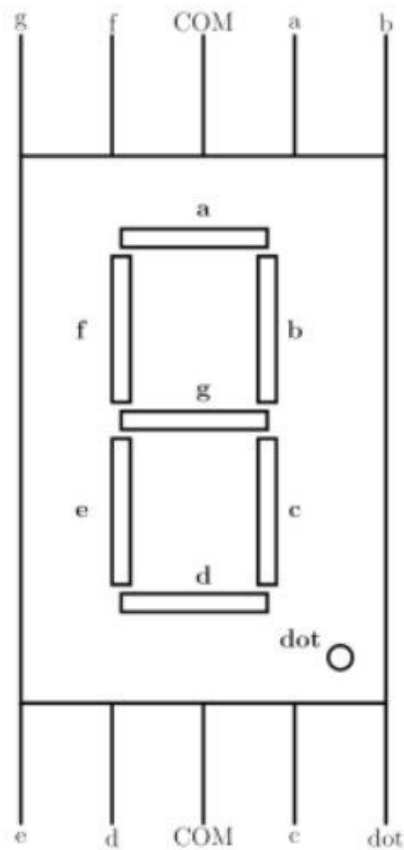


Fig. 6. Seven-segment display

- 7) Connect all the independent parts together and then connect the power source.

OUTPUT

Output was changing digits on the seven segment display the output is shown in figure 7 , 8 and 9

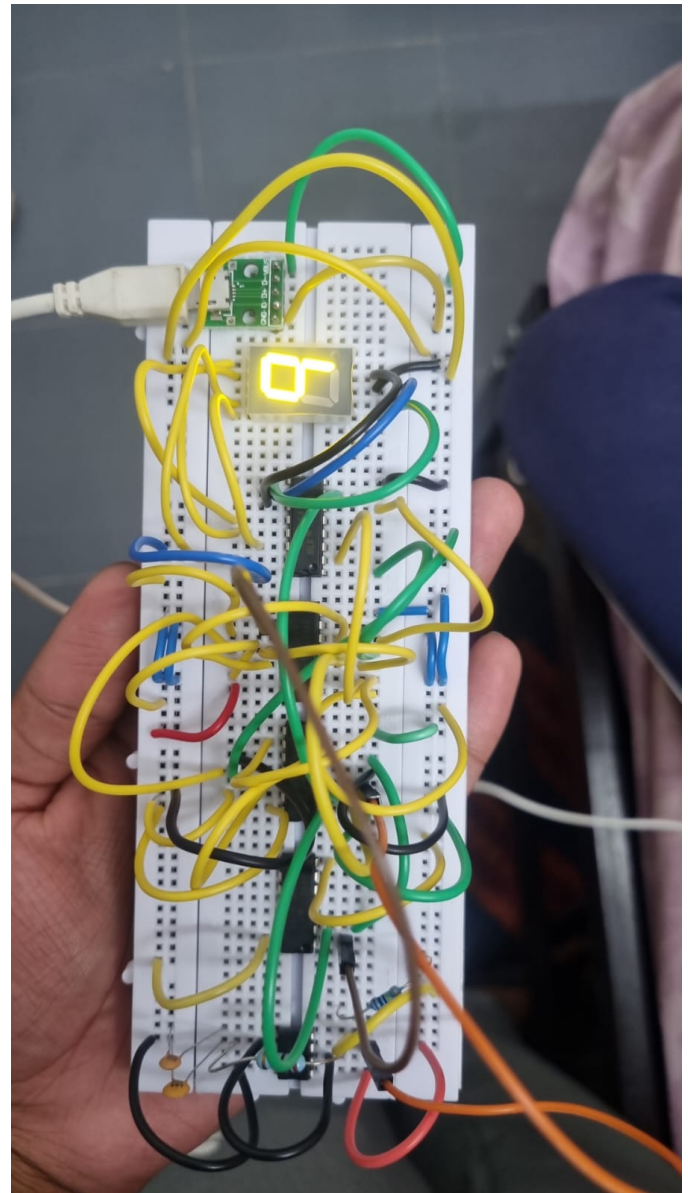


Fig. 7. Final board 1

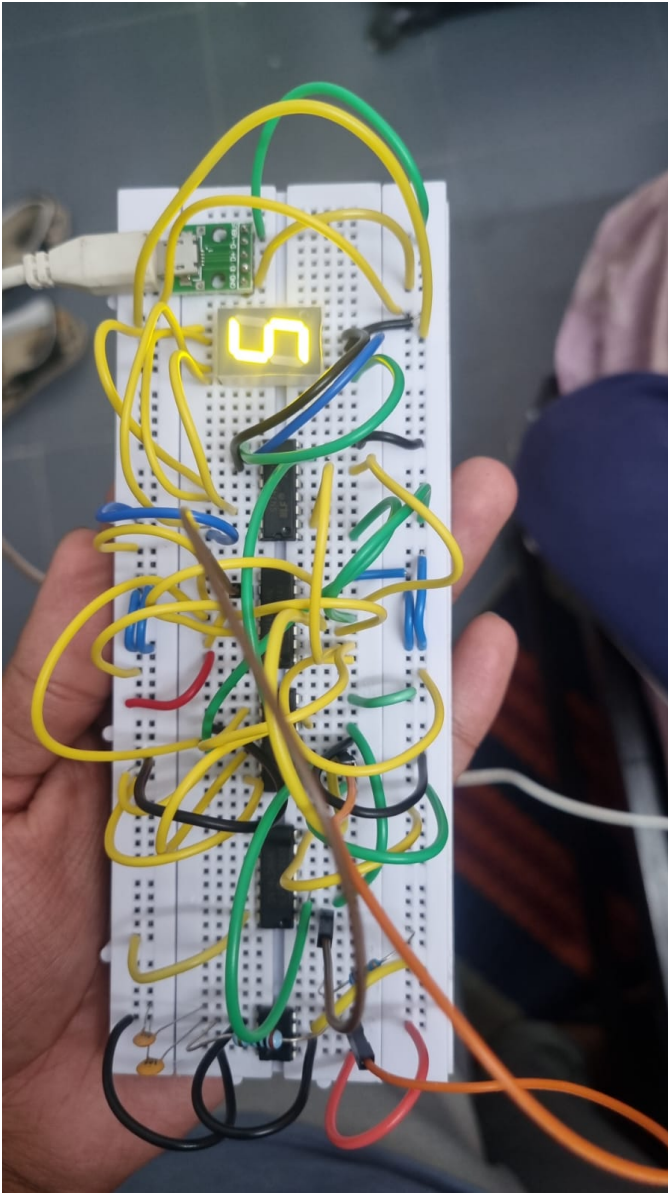


Fig. 8. Final board 2

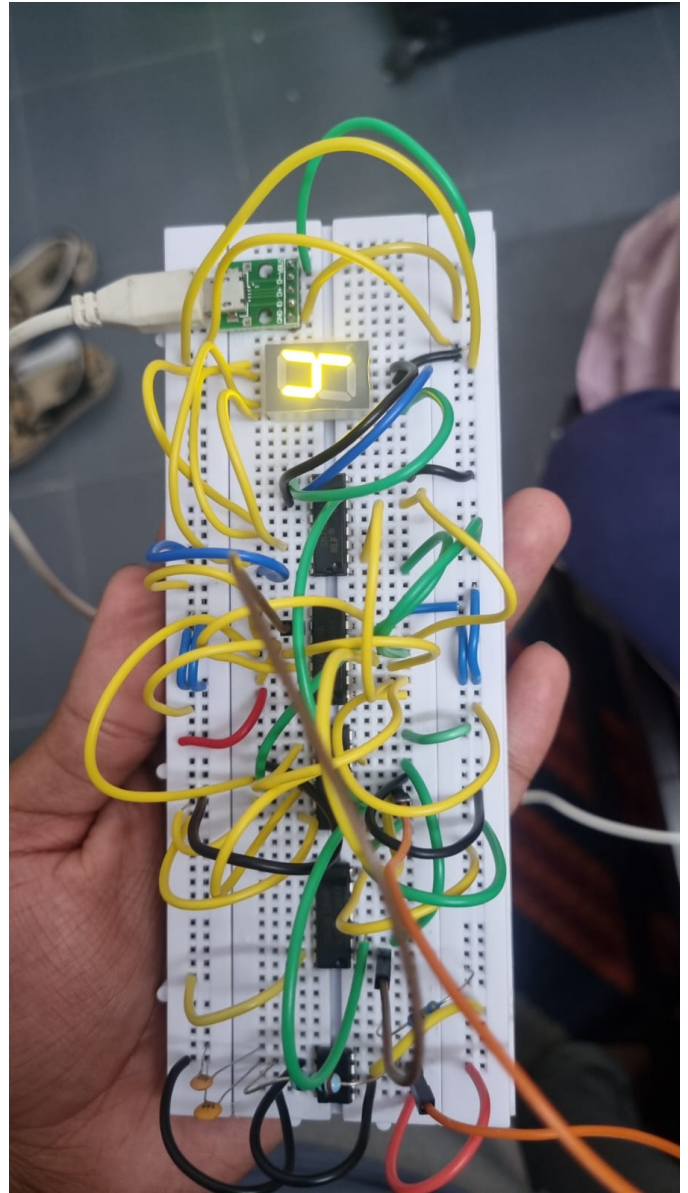


Fig. 9. Final board 3